

Sept 3rd

Note Title

03-09-2011

Performance Equation.

$$P = \frac{\text{Program}}{\text{second}} = \frac{\text{Program}}{\# \text{ insts}} \times \underbrace{\frac{\# \text{ insts}}{\# \text{ cycles}}}_{\text{IPC}} \times \underbrace{\frac{\# \text{ cycles}}{\# \text{ seconds}}}_{f}$$

Compiler      Organization      Org. + technology

$$P \propto \text{IPC} \times f$$

$f \rightarrow$  technology, design style.

IPC  $\rightarrow$  Organization.

#insts : Compiler.  
Program

---

Moore's Law: Approximately every two years  
the number of transistors double.

Power Dissipation limits frequency:

$$P \propto CV^2f$$

$$(P \propto f^3) \text{ (approx.)}$$


Temperature is a very serious problem.

Hence,

we cannot increase power

dissipation

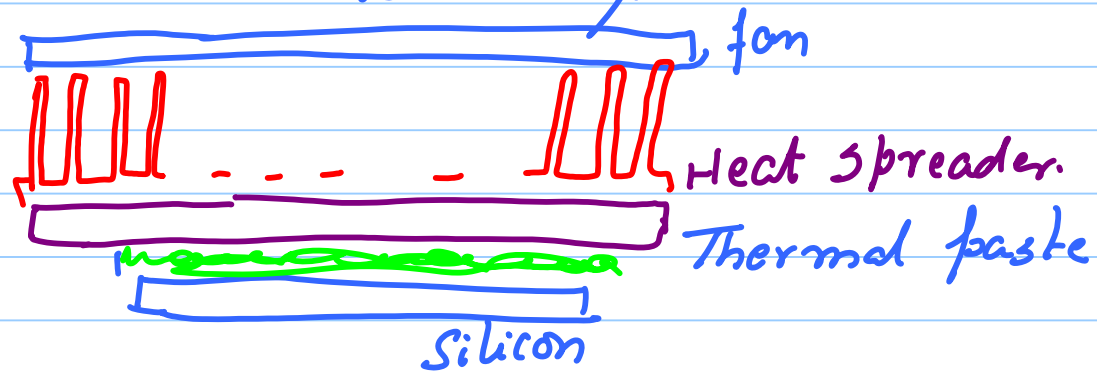High temperature  $\Rightarrow$  exponential decrease  
in reliability.



### Amdahl's Law

Any program: parallel portion ( $f$ )

$\rightarrow$  serial portion. ( $1-f$ )


$n \rightarrow$  number of processors.

$$T = 1 - f + f/n$$

$$\frac{1}{1 - 1/2 + (1/2)/n}$$

$$P = \frac{1}{T} = \frac{1}{1 - f + f/n}$$


$$f = 1/2$$

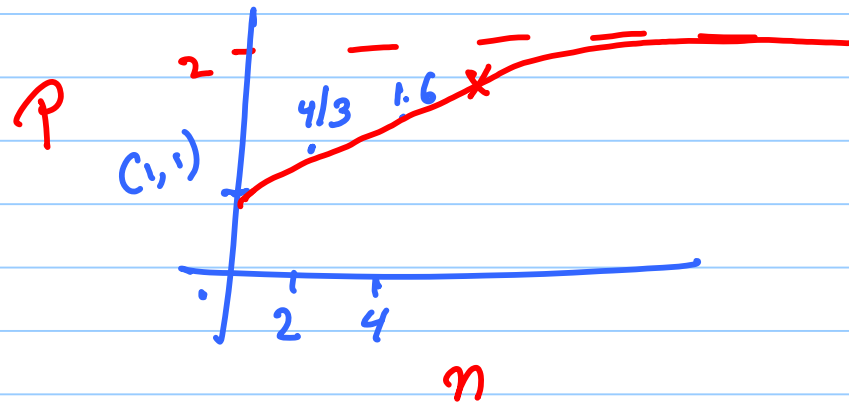

# Chapter - 3

Addition , Subtraction.


Carry Select  
Adder

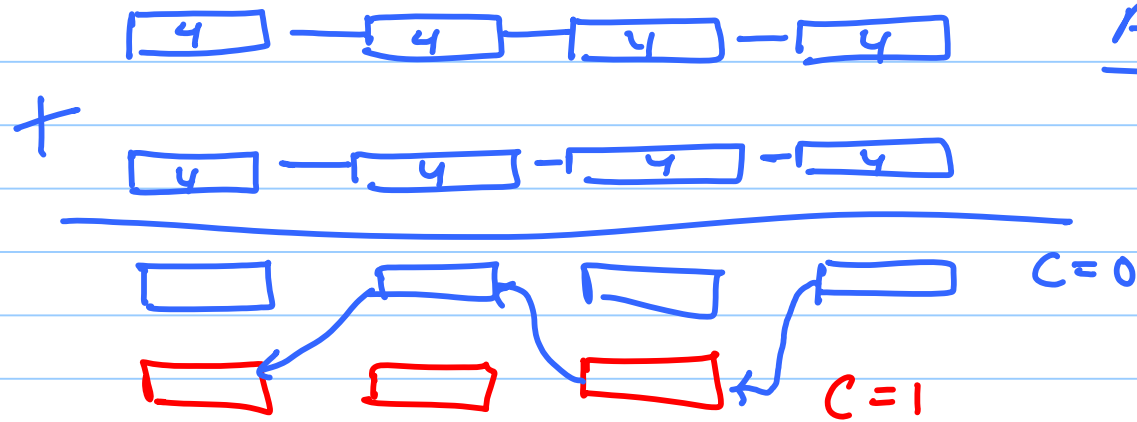

$$T = 4 + n/4$$
$$O(n)$$

Change the block size  
( $\sqrt{n}$ )
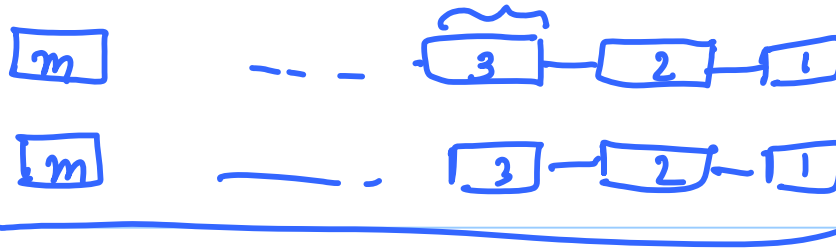
$$T = \sqrt{n} + n/\sqrt{n}$$
$$= O(\sqrt{n})$$



$$\sum_{i=1}^m i = n = O(m^2)$$

Time:  $m$  time units.


$$m = O(\sqrt{n})$$

$$m = O(\sqrt{n})$$

Time:  $O(\sqrt{n})$


# Carry Lookahead Adder

$$O(\log(n))$$

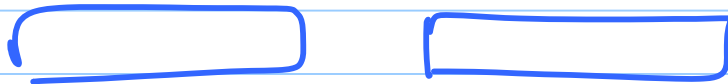


$$G = ab$$

$$P = a + b$$


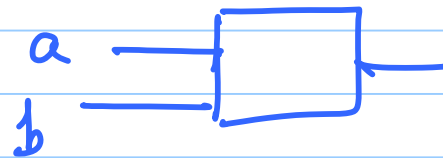


2 bit adder.

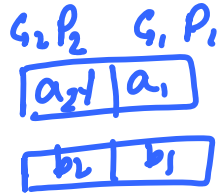

$$G = G_2 + G_1 P_2$$

$$P = P_1 P_2$$

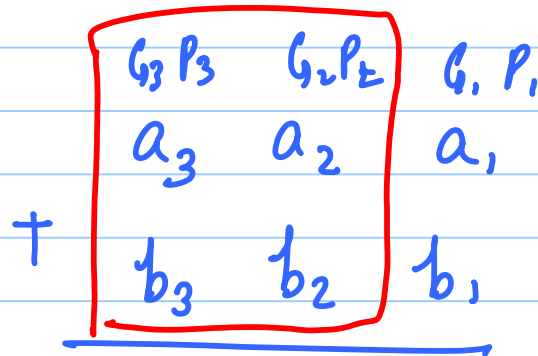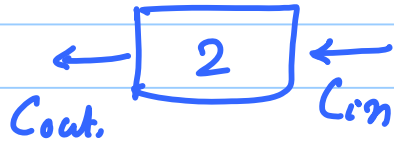

$$G = G_3 + G_2 P_3 + G_1 P_2 P_3$$

$$\tilde{P} = P_1 P_2 P_3$$

$$G_{23} = G_3 + G_2 P_3$$

$$P = P_1 P_2 P_3$$


$$P_{23} = P_2 P_3$$

$$= P_1 P_2 P_3$$


$$G = G_{23} + P_{23} G_1$$



$$= G_3 + G_2 P_3 + G_1 P_2 P_3$$

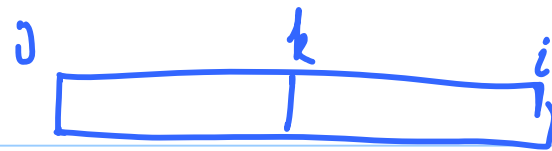




$$P_{ij} = P_{ik} P_{(k+1)j}$$

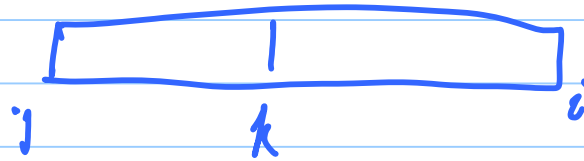

$$G_{ij} = G_{(k+1)j} + G_{ik} P_{(k+1)j}$$



$$C_{out} = G + P C_{in}$$

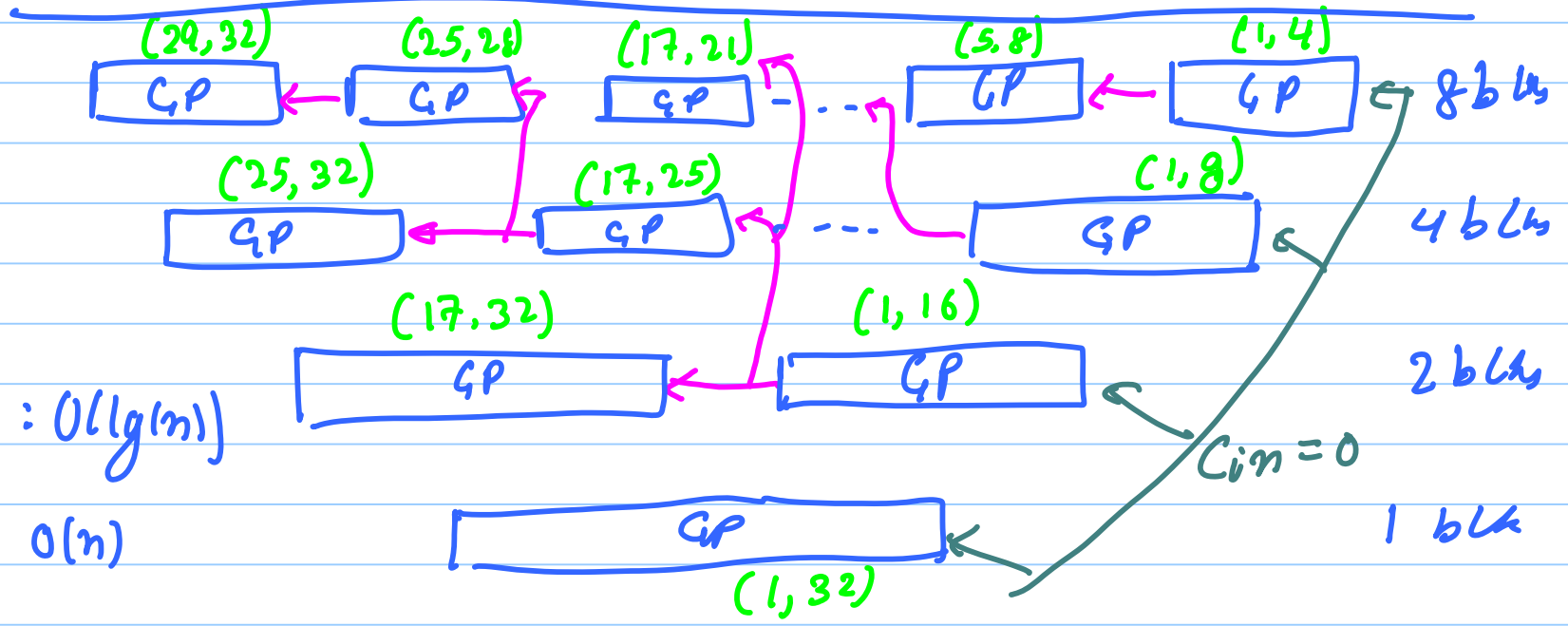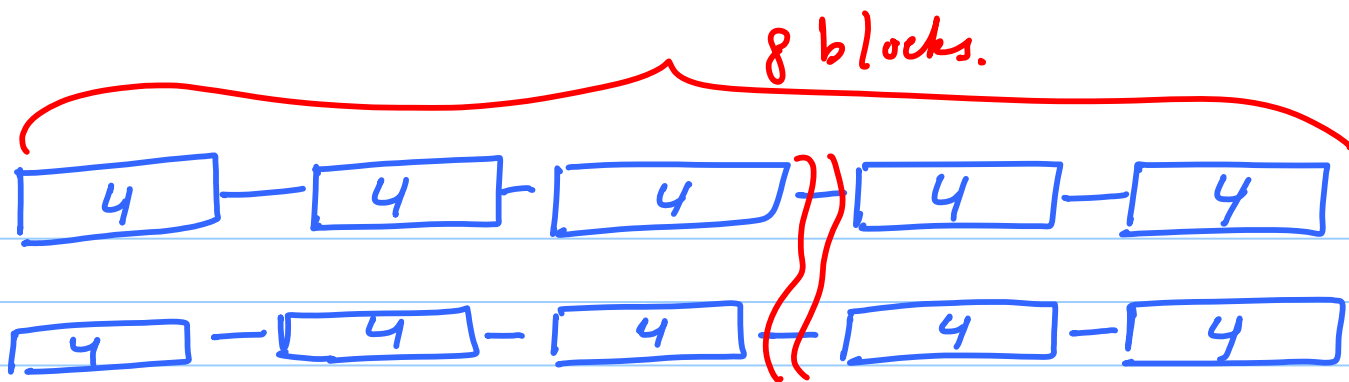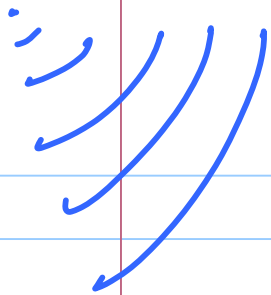

Time:  $O(\lg(n))$

Space:  $O(n)$

Optimized version of the carry

lookahead adder is called Kogge Stone adder.

Wednesday.

How long does it take to add

$m$   $n$ -bit numbers?